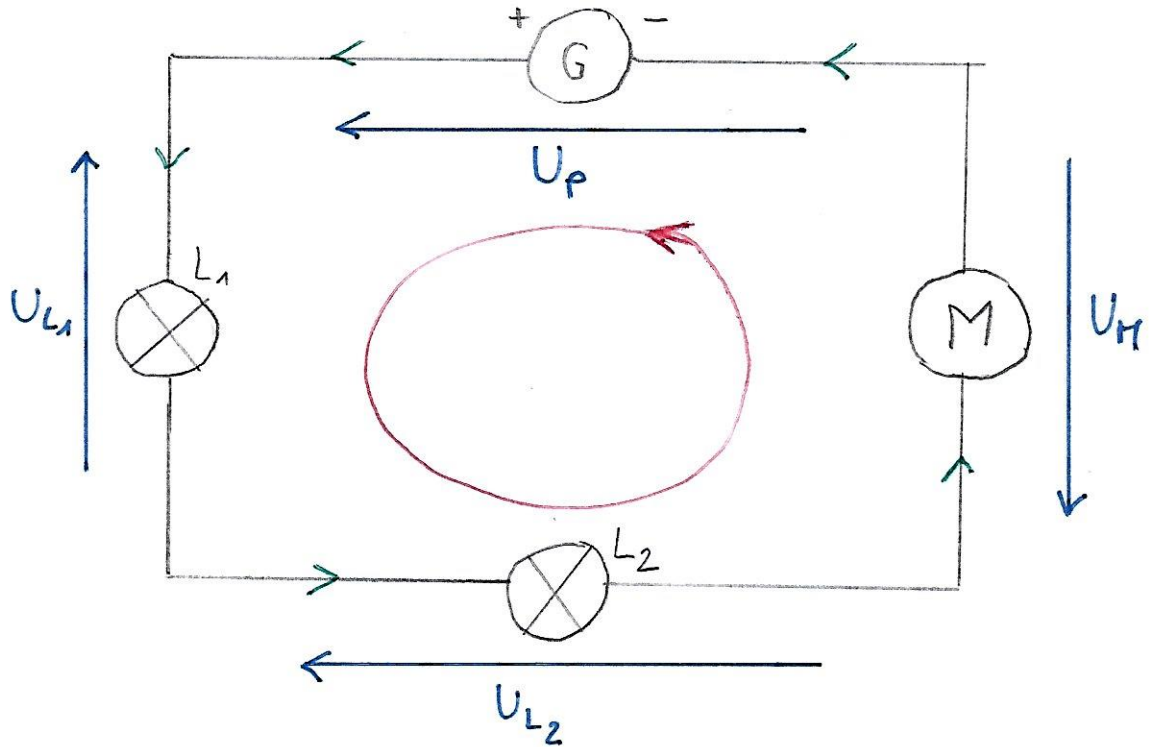


Activité 2 : loi des mailles


- 1) Doc 3: 1 maille
Doc 4: 2 mailles

2)



3)
$$U_p = U_{L_1} + U_{L_2} + U_M \quad U_p = 12,0V$$
$$2,5 + 3,5 + 6,0 = 12,0V$$

5)

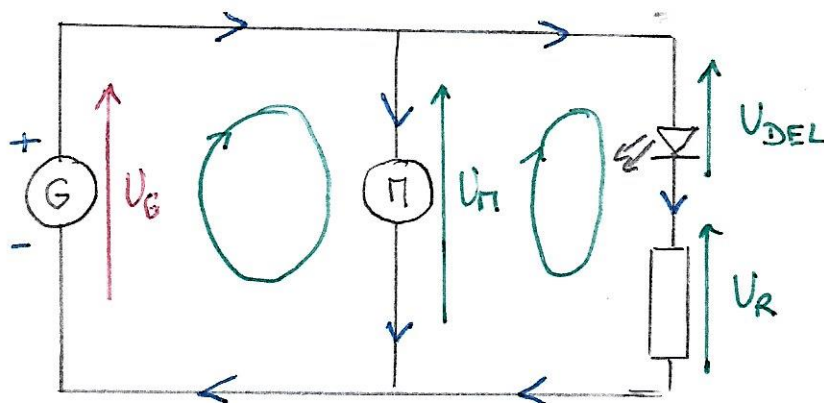

6)
$$U_G = U_M = 6,0V$$

7)
$$U_M = U_{DEL} + U_R \quad U_{DEL} = U_M - U_R = 6,0 - 4,2 = \underline{1,8V}$$